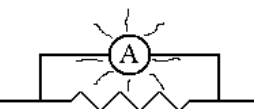


Part 1. $R_1 =$ _____ , $R_2 =$ _____ , $R_3 =$ _____ , $R_4 =$ _____
 Calculate R_{eq} :

Measured $R_{eq} =$ _____

Part 2.

ok: 

NO: 

$\mathcal{E}_1 =$ _____ , $\mathcal{E}_2 =$ _____

$R_1 =$ _____ , $R_2 =$ _____ , $R_3 =$ _____

Calculate the currents. (Work on the back or another page if necessary.)

Measured $I_1 =$ _____ , $I_2 =$ _____ , $I_3 =$ _____